

Lab 4

Registers

In this lab you will use registers in a couple of applications. The first is a register file and the second is an accumulator. You will test both applications on the FPGA board.

Part 1 (Building a register file)

Processors contain an array of registers called a register file. They are usually implemented using RAM. However, in this part, you will build a register file using regular registers with flip-flops.

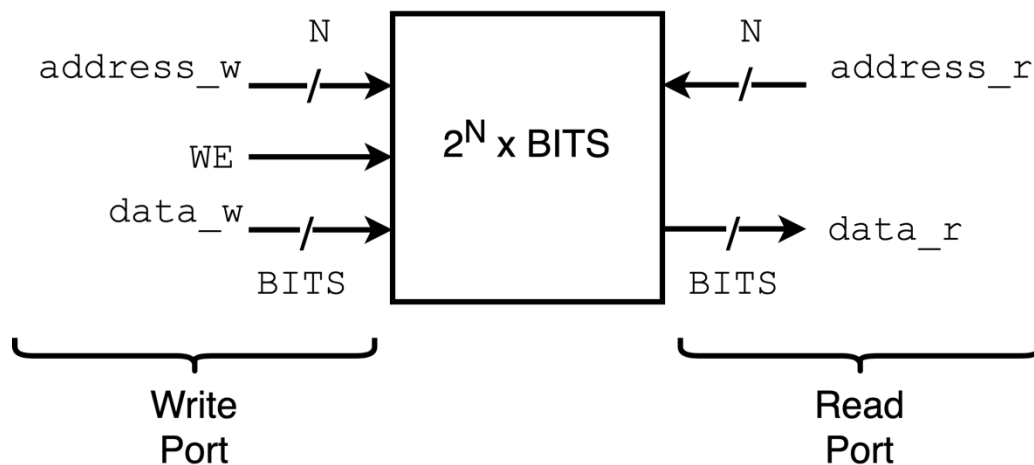


Figure 1: Register File

Figure 1 shows a register file that contains 2^N registers (rows) and each row is of size BITS (columns). This particular implementation utilizes two ports, a write port and a read port. The dual ports allow a user to access the register file for reading and writing simultaneously.

You can write a new word into the register file by placing it at `data_w` and specifying the write address on `address_w`, asserting `WE` will then invoke the write operation. A similar process can be used for reading a word from the register file, place an address on `address_r` and `data_r` will have the word stored at that address.

Generic Register File

1. Build a generic register file (call it `reg_file`) that takes two parameters `N` and `BITS`.
2. The generic register file should utilize 2^N registers and each of the registers should be of size BITS.
3. The write port can be implemented using an $N \times 2^N$ binary decoder.

4. The read port can be implemented using an $N \times 2^N$ binary decoder and a 2^N Tri-State Buffers.
5. Use the following provided code:
 - a. `simple_register_load.v` for the base registers
 - b. `decoder_generic.v` whenever you need a decoder
 - c. You need to figure out how a tri-state buffer works. *Hint:* the following implements a tri-state buffer of input a and output b
`assign b = (enable) ? a : 1'bz;`
6. Include a schematic diagram of your design with your submission

Register File Application

Verify the functionality of the register file by implementing it on the FPGA board:

1. Place your implementation in a new file called `reg_file_application.v`
2. Instantiate a version of the register file that contains 128 rows with 4 bits each.
3. `SW3` \leftarrow `SW0` should be connected to `data_w`
4. `SW10` \leftarrow `SW4` should be used to specify `address_w` or `address_r`. There isn't enough switches on the board to separate the addresses, so you will have to demultiplex them
5. `SW15` should be used to specify which address is being specified on `SW10` \leftarrow `SW4`. For example if `SW15` is `1'b1` then the address at `SW10` \leftarrow `SW4` is the read address
6. The down push button should be connected to `WE`
7. The `data_r` should be displayed on one of the seven segment digits. Use the provided `hex2sseg.v`

Question: How many Flip-Flops are being used on the board? Look at the utilizing report to figure out the answer.

Part 2 (Building an Accumulator)

Many processors contain a special function register called an accumulator (you might have seen it called a working register). The register stores the result of the last operation and might also be used in following operations.

 


Figure 2 shows a diagram of a simple accumulator that can store and accumulate the result from an adder/subtractor. Build this accumulator and test it on the FPGA board using the following specifications:

- User a 4-bit register
- Use a 4-bit adder/subtractor. You can use the provided `adder_subtractor.v`
- SW3→SW0 should be connected to input X
- SW15 should be connected to the Add/Sub input
- load should be connected to the down push button
- reset_n should be connected to the reset button
- You should display the value stored in the accumulator on one of the seven segment digits

Submission check list:

- [] All Verilog code you generated or modified
- [] All testbenches written
- [] Embed all screenshot of your testbench output in your README.md
- [] Embed all block diagram generated in your README.md
- [] Short videos demonstrating each of the parts you implemented on the FPGA